

# Exemplar examination paper

Time: 2 hours

Total: 93 marks

## Instructions


Answer all the questions.

1. Read and understand the questions before you answer.
2. Keep questions and sub-sections of the questions together.
3. Start each question on a new page.
4. Use the same numbering as indicated on the assessment.
5. Leave the margins clear for comments and mark allocation.
6. Rule off after each question.
7. Only use a black or blue ink.
8. Use  $\pi = 3,142$ .
9. All calculations must be approximated to three decimal points.

This assessment task includes a formula sheet.

## QUESTION 1: KIRCHHOFF'S LAWS

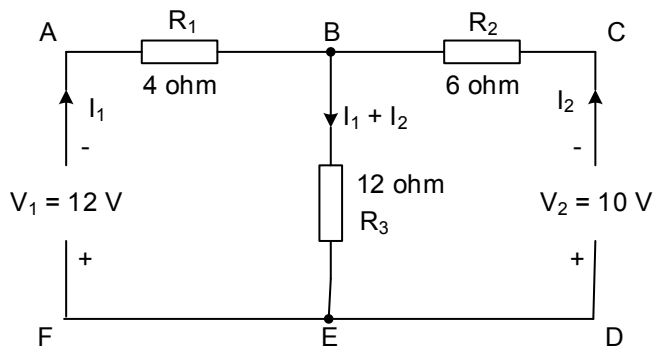- 1.1 Make use of an applicable illustration to define the following:
  - 1.1.1 Kirchhoff's Voltage Law (4)
  - 1.1.2 Kirchhoff's Current Law. (4)
- 1.2 Consider the network below and determine the magnitude of the current through resistor  $R_3$  by making use of Kirchhoff's Laws. (9)




(9)

[17]


## QUESTION 2: SUPERPOSITION THEOREM

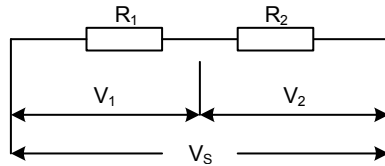- 2.1 Consider the network below and only give the mathematical expressions that can be used to calculate the voltage across  $R_1$  and  $R_2$ .



(4)

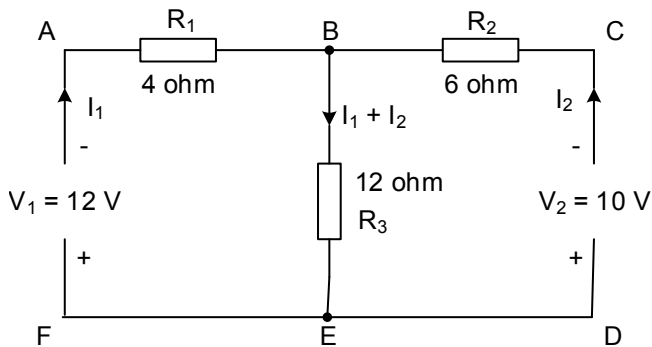- 2.2 Consider the network below and determine the magnitude of the current through resistor  $R_3$  by making use of the Superposition Theorem.




(9)

[13]

## QUESTION 3: THEVENIN'S THEOREM

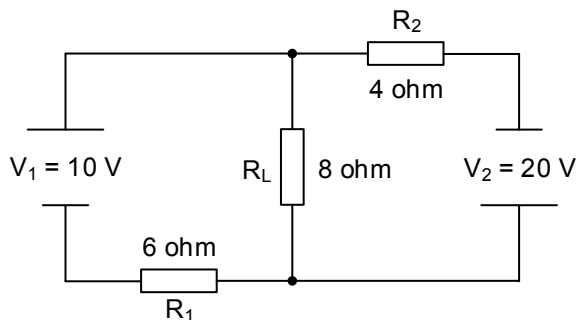- 3.1 Define Thevenin's Theorem. (3)
- 3.2 Consider the network below and determine the magnitude of the current through resistor  $R_L$  by making use of Thevenin's Theorem.




(11)

[14]

### QUESTION 4: SERIES RLC NETWORKS

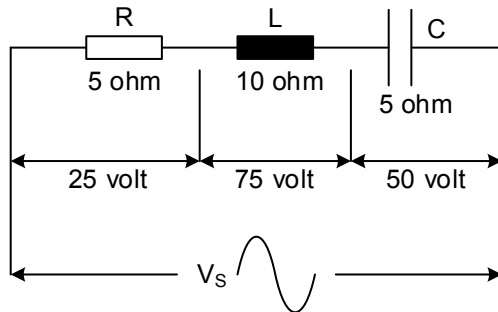4.1 Consider the network below and determine the following quantities.



4.1.1 The impedance of the network; (3)

4.1.2 The magnitude of the supply voltage; and (3)


4.1.3 The phase angle between the line current and supply voltage. You are also required to state whether the line current is leading or lagging. Motivate your answer! (4)

4.2 Draw a neat labelled graphic representation that will illustrate the concept of resonance. (3)

[13]

### QUESTION 5: PARALLEL RLC NETWORKS

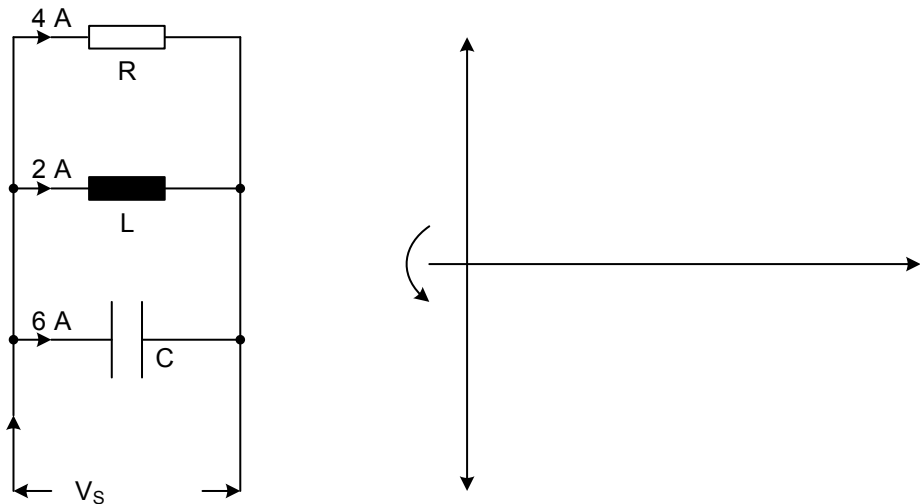5.1 Consider figure 5 on the answer sheet and complete the phasor diagram. You are further required to determine the total line current.



(7)

- 5.2 Draw neat, labelled graphical representations that will illustrate:
- 5.2.1 Current versus frequency in a parallel RLC resonant network; and (4)
  - 5.2.2 Frequency versus impedance in a parallel RLC resonant network (4)
- [15]

**QUESTION 6: Q-FACTOR, BANDWIDTH AND COMPLEX NOTATION**

- 6.1 Give another term for Q-factor. (1)
  - 6.2 Define bandwidth. (3)
  - 6.3 A series RLC network consists of a resistor having a value of 12 ohm, an inductor having a value of 0,15 Henry and a capacitor having a value of 100  $\mu$ -Farad connected across a 100 V/50 Hz alternating supply. Use complex notation and calculate the:
    - 6.3.1 Total impedance of the network; (8)
    - 6.3.2 Total line current in the network; and (3)
    - 6.3.3 Voltage drops across the inductor and capacitor. (6)
- [21]

**TOTAL: 93 marks**

# Formula sheet

## Kirchhoff's Laws

$$V_R = I_1 \times R$$

$$P_R = I_2^2 \times R$$

## Thevenin's Theorem

$$V_R = I_1 \times R \quad P_R = I_2^2 \times R$$

## Maximum power transfer

$$I_L = \frac{V_s}{R_s + R_L} \quad P_L = I_L^2 \times R_L$$

## RLC-networks

Resistor

$$I = \frac{V_s}{R} \quad R = \frac{V_s}{I}$$

$$V_s = I \times R$$

Inductor

$$X_L = 2 \times \pi \times f \times L$$

$$I_L = \frac{V_s}{X_L} \quad V_L = I_L \times X_L$$

$$X_L = \frac{V_s}{I_L}$$

Capacitor

$$X_C = \frac{1}{2 \times \pi \times f \times C}$$

$$I_C = \frac{V_s}{X_C} \quad V_C = I_C \times X_C$$

$$X_C = \frac{V_s}{I_C}$$

## Series RL-network

$$Z = \sqrt{R^2 + X_L^2}$$

$$V_s = \sqrt{V_R^2 + V_L^2}$$

$$V_R = I \times R \quad V_L = I \times X_L$$

$$I = \frac{V_s}{Z}$$

## Superposition Theorem

Current division

$$I_1 = \frac{R_2}{R_1 + R_2} \times I_T \quad I_2 = \frac{R_1}{R_1 + R_2} \times I_T$$

Voltage division

$$V_1 = \frac{R_1}{R_1 + R_2} \times V_s \quad V_2 = \frac{R_2}{R_1 + R_2} \times V_s$$

$$V_R = I_1 \times R \quad P_R = I_2^2 \times R$$

## Norton's Theorem

$$V_R = I_1 \times R \quad P_R = I_2^2 \times R$$

## Series RC-network

$$Z = \sqrt{R^2 + X_C^2}$$

$$V_s = \sqrt{V_R^2 + V_C^2}$$

$$V_R = I \times R \quad V_C = I \times X_C$$

$$I = \frac{V_s}{Z}$$

$$\theta = \tan^{-1} \frac{X_L}{R}$$

$$\theta = \tan^{-1} \frac{V_L}{V_R}$$

$$\theta = \tan^{-1} \frac{X_C}{R}$$

$$\theta = \tan^{-1} \frac{V_C}{V_R}$$

### Series RLC-network

$$Z = \sqrt{R^2 + (X_C \sim X_L)^2}$$

$$V_S = \sqrt{V_R^2 + (V_C \sim V_L)^2}$$

$$V_C = I \times X_C$$

$$V_R = I \times R$$

$$V_L = I \times X_L$$

$$I = \frac{V_S}{Z}$$

$$\cos \theta = \frac{R}{Z}$$

$$\theta = \cos^{-1} \frac{R}{Z}$$

True power =  $V \times I \cos \theta$  watt

Apparent power =  $V \times I$  watt

### Parallel RL-network

$$Z = \frac{R \times X_L}{\sqrt{R^2 + X_L^2}}$$

$$Z = \frac{V_S}{I_T}$$

$$I_T = \sqrt{I_R^2 + I_L^2}$$

$$I_L = \frac{V_S}{X_L}$$

$$I_R = \frac{V_S}{R}$$

$$\theta = \tan^{-1} \frac{I_L}{I_R}$$

$$\theta = \cos^{-1} \frac{I_R}{I_T}$$

### Parallel RLC-network

$$Z = \frac{1}{\sqrt{R^2 + (\frac{1}{X_C} \sim \frac{1}{X_L})^2}}$$

$$Z = \frac{V_S}{I_T}$$

$$I_T = \sqrt{I_R^2 + (I_C \sim I_L)^2}$$

$$I_C = \frac{V_S}{X_C}$$

$$I_R = \frac{V_S}{R}$$

$$I_T = \frac{V_S}{Z}$$

$$\theta = \tan^{-1} \frac{I_C}{I_R}$$

$$\theta = \cos^{-1} \frac{I_R}{I_T}$$

### Parallel RC-network

$$Z = \frac{R \times X_C}{\sqrt{R^2 + X_C^2}}$$

$$Z = \frac{V_S}{I_T}$$

$$I_T = \sqrt{I_R^2 + I_C^2}$$

$$I_L = \frac{V_S}{X_C}$$

$$I_R = \frac{V_S}{R}$$

$$\theta = \tan^{-1} \frac{I_C}{I_R}$$

$$\theta = \cos^{-1} \frac{I_R}{I_T}$$

### Tuned circuit (tank circuit)

$$f = \frac{1}{2 \times \pi \times \sqrt{L \times C}}$$

$$Z_D = \frac{L}{R \times C}$$

$$I_L = \frac{V_S}{X_L}$$

$$I_T = \frac{V_S}{Z}$$

$$I_L = \frac{V_S}{X_L}$$

$$I_C = \frac{V_S}{X_C}$$

## Q-factor, bandwidth and complex notation

$$Q = \frac{X_L}{R} \quad \text{or} \quad Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$X_L = j2 \times \pi \times f \times L$$

$$X_C = \frac{-j1}{2 \times \pi \times f \times C}$$

at resonance

$$Q = \frac{X_C}{R} \quad Q = \frac{X_L}{R}$$

$$Z = R + j$$

$$Z = R - j$$

$$I = \frac{V}{Z}$$

$$V_L \text{ or } V_C = V_s \times Q$$

$$V_L = I \times X_L$$

$$V_C = I \times X_C$$

$$V_R = I \times R$$


$$I_L \text{ or } I_C = I_T \times Q$$

$$BW = \frac{R}{2 \times \pi \times L} \quad \text{or} \quad BW = \frac{fr}{Q}$$

# Exemplar examination paper memorandum


## QUESTION 1: KIRCHHOFF'S LAWS

1. 1.1 1.1.1

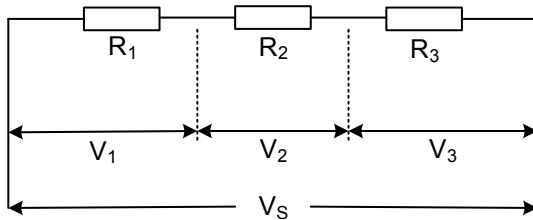


The algebraic sum ✓ of the individual voltage drops ✓ in a network is equal to the algebraic sum ✓ of the applied voltage. ✓

1.1.2

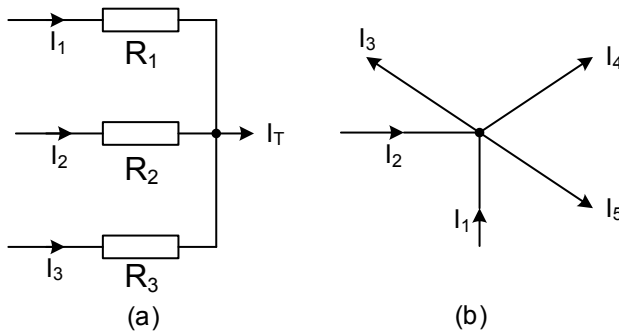

Kirchhoff's Current Law states that the algebraic sum ✓ of currents entering a point will be equal ✓ to the algebraic sum ✓ of the currents leaving that point. ✓

1.2

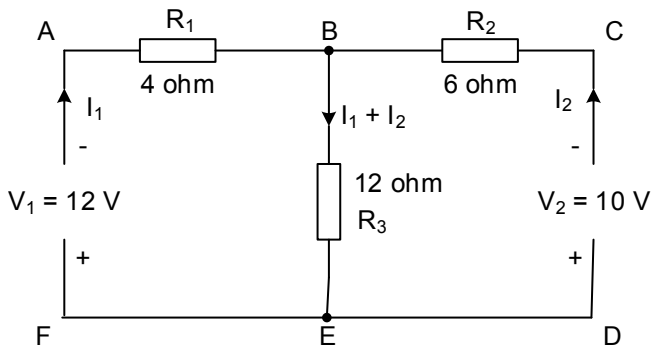



**Loop ABEFA**

$$R_1 I_1 + R_3(I_1 + I_2) = V_1$$

$$4I_1 + 12(I_1 + I_2) = 12$$

$$4I_1 + 12I_1 + 12I_2 = 12$$

$$16I_1 + 12I_2 = 12 \quad (1) \checkmark$$

$$(1) \times 12: 192I_1 + 144I_2 = 144 \quad (3) \checkmark$$

$$(2) \times 16: 192I_1 + 288I_2 = 160 \quad (4) \checkmark$$

$$(3) - (4): \frac{-144I_2}{-144I_2} = \frac{-16}{-144I_2}$$

$$I_2 = 0,111 \text{ A} \checkmark$$

Substitute  $I_2 = 0,111 \text{ A}$  in (1)

$$8I_1 + 6I_2 = 12 \checkmark$$

$$8I_1 + 6(0,111) = 12 \checkmark$$

$$8I_1 + 0,666 = 12$$

$$I_1 = 1,417 \text{ A} \checkmark$$

**Loop CBEDC**

$$R_2 I_2 + R_3(I_1 + I_2) = V_2$$

$$6I_2 + 12(I_1 + I_2) = 10$$

$$6I_2 + 12I_1 + 12I_2 = 10$$

$$12I_1 + 18I_2 = 10 \quad (2) \checkmark$$

$$I_{R3} = I_1 + I_2$$

$$= 1,417 + 0,111$$


$$= 1,528 \text{ A} \checkmark$$

**QUESTION 2: SUPERPOSITION THEOREM**

2. 2.1  $V_1 = \frac{R_1}{R_1 + R_2} \times V_s \checkmark \checkmark$

$V_2 = \frac{R_2}{R_1 + R_2} \times V_s \checkmark \checkmark$

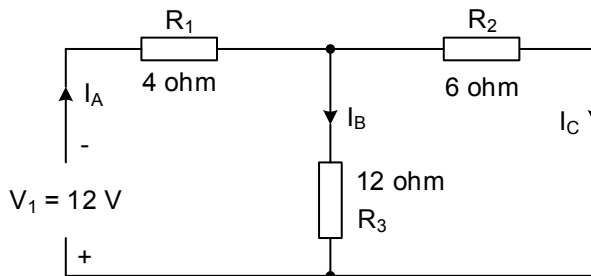2.2 Short circuit  $V_2$ , indicate current direction and calculate values.  $\checkmark$



$$R_{TA} = R_1 + \frac{R_2 \times R_3}{R_2 + R_3}$$

$$= 4 + \frac{6 \times 12}{6 + 12}$$

$$= 8 \text{ ohm} \checkmark$$

$$I_A = \frac{V_1}{R_{TA}}$$

$$= \frac{12}{8}$$


$$= 1,5 \text{ A} \checkmark$$

$$I_B = \frac{R_2}{R_2 + R_3} \times I_A$$

$$= \frac{6}{6 + 12} \times 1,5$$

$$= 0,5 \text{ A} \checkmark$$

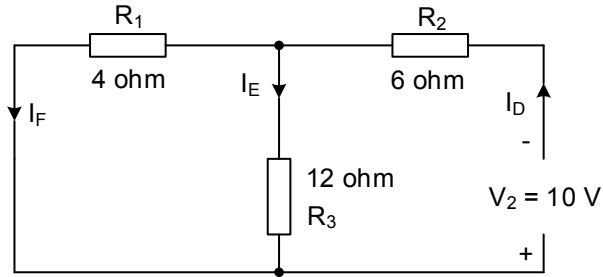Replace  $V_2$  and short circuit  $V_1$ , indicate current direction and calculate values. ✓



$$R_{TA} = R_2 + \frac{R_1 \times R_3}{R_1 + R_3}$$

$$I_D = \frac{V_2}{R_{TA}}$$

$$= 6 + \frac{4 \times 12}{4 + 12}$$

$$= \frac{10}{9}$$

$$= 9 \text{ ohm } \checkmark$$

$$= 1,111 \text{ A } \checkmark$$

$$I_E = \frac{R_1}{R_1 + R_3} \times I_D$$

$$= \frac{4}{4 + 12} \times 1,111$$

$$= 0,278 \text{ A } \checkmark$$


Since  $I_B$  and  $I_E$  are in the same direction through  $R_3$  they can be added together:

$$I_B + I_E = 0,5 + 0,278 = 0,778 \text{ A } \checkmark$$


### QUESTION 3: THEVENIN'S THEOREM

3. 3.1 A complex network consisting of impedances and voltage sources ✓ may be replaced by a constant voltage source ✓ with series impedance. ✓

3.2

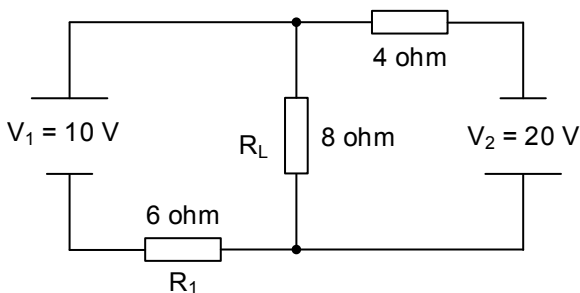

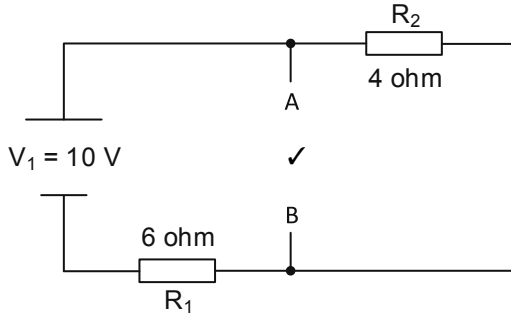Short circuit  $V_2$ , remove  $R_L$  and mark terminal A and B. ✓




$$V_{TH1} = \frac{R_2}{R_1 + R_2} \times V_1$$

$$= \frac{4}{6 + 4} \times 10$$

$$= 4 \text{ volt } \checkmark$$

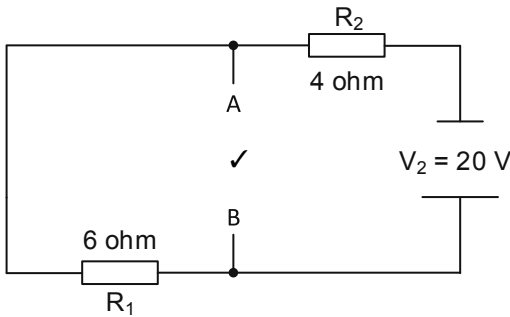Replace  $V_2$ , Short circuit  $V_1$ . ✓



$$V_{TH2} = \frac{R_1}{R_1 + R_2} \times V_2$$


$$= \frac{6}{4 + 6} \times 20$$

$$= 12 \text{ volt } \checkmark$$

$$V_{THT} = V_{TH2} - V_{TH1}$$

$$= 12 - 4$$

$$= 8 \text{ volt } \checkmark$$

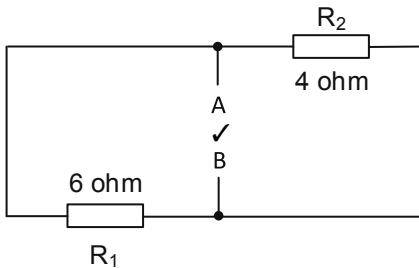


$$R_{TH} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$= \frac{6 \times 4}{6 + 4}$$

$$= 2,4 \text{ ohm} \checkmark$$

### Equivalent network

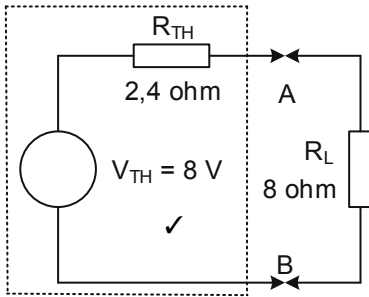

$$I_{RL} = \frac{V_{THT}}{R_{TH} + R_L}$$

$$= \frac{8}{2,4 + 8}$$

$$= 0,769 \text{ ampere} \checkmark$$

### QUESTION 4: SERIES RLC NETWORKS

4. 4.1 4.1.1  $Z = \sqrt{R^2 + (X_L - X_C)^2} \checkmark$

$$= \sqrt{5^2 + (10 - 5)^2} \checkmark$$

$$= 7,071 \text{ ohm} \checkmark$$

4.1.2  $V_S = \sqrt{V_R^2 + (V_L - V_C)^2} \checkmark$


$$= \sqrt{25^2 + (75 - 50)^2} \checkmark$$

$$= 35,355 \text{ volt} \checkmark$$

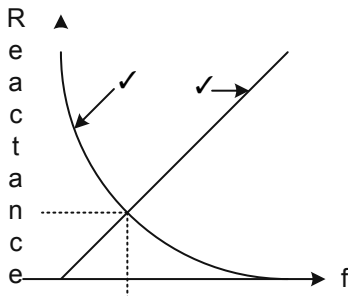4.1.3  $\theta = \cos^{-1} \frac{R}{Z} \checkmark$


$$= \cos^{-1} \frac{5}{7,071} \checkmark$$

$$= 44,999^\circ \text{ leading since } V_L > V_C \checkmark$$




## QUESTION 5: PARALLEL RLC NETWORKS

5. 5.1

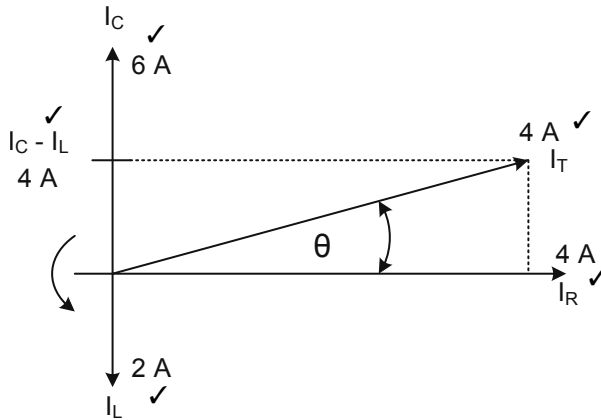


$$\begin{aligned}
 I_T &= \sqrt{I_R^2 + (I_C - I_L)^2} \checkmark \\
 &= \sqrt{4^2 + (6 - 2)^2} \checkmark \\
 &= 4 \text{ ampere} \checkmark
 \end{aligned}$$

5.2 5.2.1

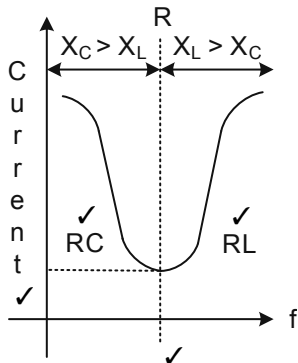

5.2.2

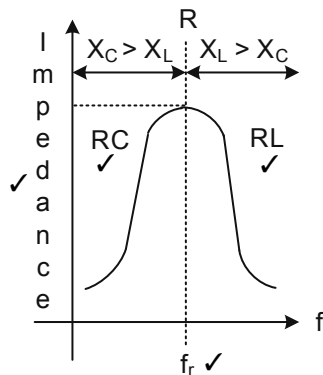

## QUESTION 6: Q-FACTOR, BANDWIDTH AND COMPLEX NOTATION

6. 6.1 Magnification factor ✓  
6.2 Bandwidth is that range of frequencies ✓ between two points ✓ where the power has fallen to half of its value. ✓

$$\begin{aligned}6.3 \quad 6.3.1 \quad X_L &= 2 \times \pi \times f \times L \quad \checkmark \\ &= 2 \times 3,142 \times 50 \times 0,15 \\ &= 47,13 \text{ ohm} \quad \checkmark\end{aligned}$$

$$\begin{aligned}X_C &= 1 \quad \checkmark \\ &= 2 \times \pi \times f \times C \\ &= \frac{1}{2 \times 3,142 \times 50 \times 200 \times 10^{-6}} \\ &= 15,913 \text{ ohm} \quad \checkmark\end{aligned}$$

$$\begin{aligned}Z &= R + j(X_L - X_C) \quad \checkmark \\ &= 12 + j(47,13 - 15,913) \quad \checkmark \\ &= 12 + j31,217 \text{ ohm} \quad \checkmark \\ &= 33,44 \angle 69^\circ \text{ ohm} \quad \checkmark\end{aligned}$$

$$\begin{aligned}6.3.2 \quad I_T &= \frac{V}{Z} \quad \checkmark \\ &= \frac{200 \angle 0^\circ}{33,44 \angle 69^\circ} \quad \checkmark \\ &= 5,98 \angle -69^\circ \text{ ampere} \quad \checkmark\end{aligned}$$

$$\begin{aligned}6.3.3 \quad V_L &= I_T \times X_L \quad \checkmark \\ &= 5,98 \angle -69^\circ \times 47,13 \angle 90^\circ \quad \checkmark \\ &= 281,737 \angle 21^\circ \text{ volt} \quad \checkmark\end{aligned}$$

$$\begin{aligned}V_C &= I_T \times X_C \quad \checkmark \\ &= 5,98 \angle -69^\circ \times 15,913 \angle -90^\circ \quad \checkmark \\ &= 95,16 \angle -159^\circ \text{ volt} \quad \checkmark\end{aligned}$$